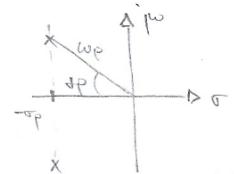


CSE

# Summary 2021 - Noah flutter

## U: Intro

Poles &amp; zeros



$$T(s) = \frac{N(s)}{D(s)} = \dots = \frac{\dots}{(s^2 + \frac{w_p}{q_p}s + w_p^2)} \dots$$

Any poly can be factored into terms of order 1 & 2 w/ real coefficients

$$q_p = \frac{w_p}{2\omega_p} \quad 2q_p = \frac{w_p}{\omega_p} = \frac{1}{\cos \phi_p}$$

$$H(s) = \frac{N(s)}{s^2 + \frac{w_p}{q_p}s + w_p^2}$$




$$N(s) = \begin{cases} K \omega_0 & LP \\ K \frac{\omega_0}{q_p} s & BP \\ K(w_p - s^2) & BR \text{ (notch)} \\ K s^2 & HP \end{cases}$$

2nd order  
1st order

$$H(s) = \frac{K_1 s + K_0}{s + \omega_0} \quad \begin{cases} \omega_0 = 0 & HP \\ \omega_0 \neq 0 & LP \end{cases}$$

$$H(s) = \frac{b^1 2 D \omega_p s}{s^2 + 2 D \omega_p s + w_p^2}$$
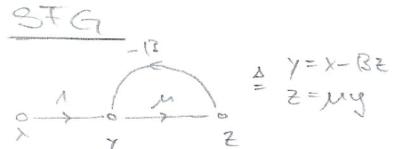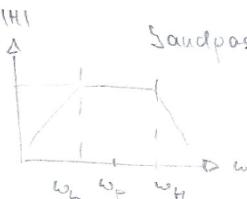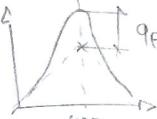
$$B = 2 D f_p = f_u - f_L \quad q_p = \frac{1}{2D}$$



$$G = \frac{z}{x} = \frac{\sum \Delta_i p_i}{\Delta}$$

$\Delta = 1 - \text{sum of all loops}$   
 $+ \text{sum of prod. of all comb. of two loop that have no nodes in common}$   
 $- \text{sum of three ...} + \dots$

$p_i = \text{forward paths}$   
 $\Delta_i = \Delta \text{ with terms removed that touch } p_i$

The STG establishes relationship between variables. Causality comes only from source superposition (e.g. z is controlled by y)

- DPSFG
- Add magic sources where no source exists already
  - Draw driving-point impedances
  - Draw imp. & opp.
  - Draw active devices
  - Draw passive devices
  - Add currents where required
  - Mason!

1

## Graphical Manipulations

$$\begin{array}{lcl} \text{Diagram 1} & = & \text{Diagram 2} \\ \text{Diagram 3} & = & \text{Diagram 4} \\ \text{Diagram 5} & = & \text{Diagram 6} \\ \text{Diagram 7} & = & \text{Diagram 8} \end{array}$$

$$\begin{array}{lcl} \text{Diagram 9} & = & \text{Diagram 10} \\ \text{Diagram 11} & = & \text{Diagram 12} \\ \text{Diagram 13} & = & \text{Diagram 14} \\ \text{Diagram 15} & = & \text{Diagram 16} \\ \text{Diagram 17} & = & \text{Diagram 18} \\ \text{Diagram 19} & = & \text{Diagram 20} \end{array}$$


→ check units ( $I \rightarrow V_{out}$ , ...)

## STG Impedances

**Input:**  
- Write lin. node eqn  
- Solve  $\frac{1}{Z_{in}} = \frac{I_{in}}{V_{in}}$

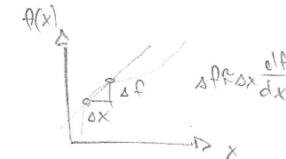**Output**

- Inject test current  $I_{test}$   
- Solve for  $Z_{out} = \frac{V_{out}}{I_{test}}$



## Sensitivity

$$S_x = \frac{df}{dx} \cdot \frac{x}{f}$$

$\% \Delta f \approx \% x \cdot \frac{df}{dx} \cdot \frac{x}{f} = \% x \cdot S_x$

change of x in percent


## L2: Gm-C filters

$$V_c(t) = \frac{1}{C} \int i_C(t) dt$$

## Integrator-Loop Filters

$$\text{Need } D(s) = s^2 + \frac{w_p}{q_p}s + w_p^2, \text{ with integrator: } \Delta = \frac{D(s)}{s^2} = \frac{w_p}{s^2} + \frac{1}{q_p s} + \frac{w_p^2}{s^2}$$

For LP/BP/HP:

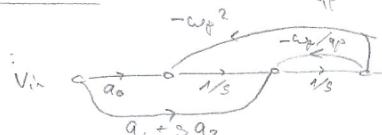


$$\frac{Q_2 s^2 + Q_1 s + Q_0}{s^2 + \frac{w_p}{q_p}s + w_p^2}$$

1st problem:  $\frac{1}{s}$  -> opamp implement → scale fc2nd problem:  $\frac{1}{s}$  -> convert 1 to V → OTA V


$$I = g_m \cdot V \quad \text{Operational Transconductance Amplifier}$$

## Gm-C Biquad

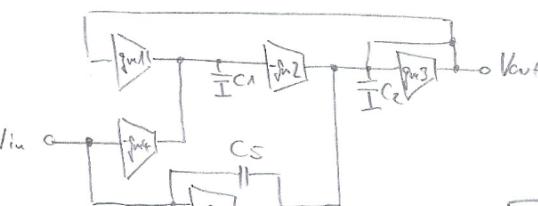

2

## Op-Amp Integration

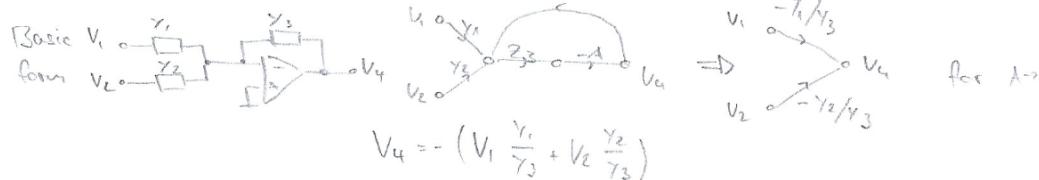

poles of  $\hat{d} \Rightarrow s = \frac{-a_1 \pm \sqrt{a_1^2 - 4a_2a_0}}{2a_2}$ ,  $a_1^2 \geq 4a_2a_0$

and  $\hat{d} - A u_{32}$  should have complex poles:

I)  $\hat{a}_{32} \rightarrow A < 0$ ,  $u_{32} = b_0$

II)  $\hat{a}_{32} \rightarrow A < 0$ ,  $u_{32} = b_2 s^2$

III)  $\hat{a}_{32} \hat{a}_{12} \rightarrow A < 0$ ,  $u_{32} = b_2 s^2 + b_0$

IV)  $\hat{a}_{32} \rightarrow A > 0$ ,  $u_{32} = b_1 s$

LP


HP } very gain amp

BR } only one works with  $A \rightarrow \infty$


BP } res. gain amp

## Gm-C voice


Physically, noise is generated at output

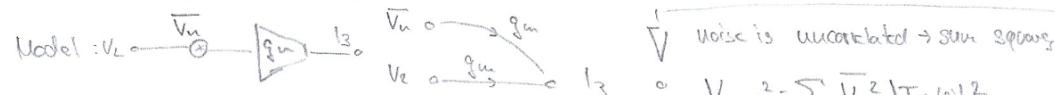

## Non-ideal Gm-C

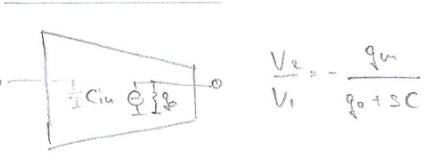

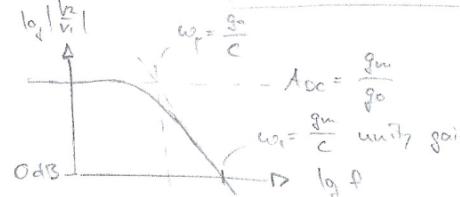
$$\frac{V_L}{V_1} = -\frac{g_m}{g_o + SC}$$




- Cm parallel to signal cap C  $\rightarrow C_m \cdot C_m \ll 1$
- $g_o$  sets  $\omega_p$  and gain. All caps must be lower than freq. of interest
- $g_m(s)$  has a phase lag  $\rightarrow$  stability problems!

## Balanced Circuit

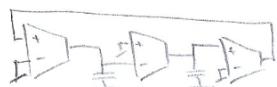

$\Rightarrow$

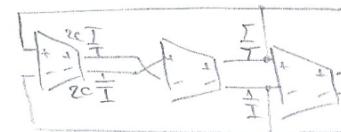

better power supply  
noise rejection

## L3: Op-Amp-RC-Filter


### SAB (Single Amp Biquad)

Gm-C difficult to realize linear.

High-gain opamp are better.

Opamp less sensitive on 3-amp filter.
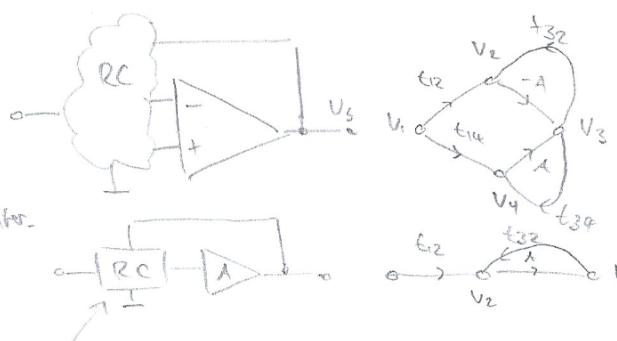
$$T = \frac{A(t_{12} - t_{14})}{A + A u_{32} - A t_{34}} = \frac{t_{12} - t_{14}}{t_{22} - t_{34}}$$




If feed & fb path go through same net:  $t_{12} = \frac{b_{12}}{d}$   $t_{32} = \frac{b_{32}}{d} \rightarrow d = 0_1 s^2 + a_1 s + a_0$   
 $d$  can't have complex poles  $\rightarrow$  require feedback

$$T = \frac{A u_{32}}{d - A u_{32}}$$

[3]

## Ackerberg-Nossler

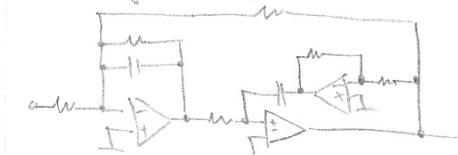

more robust to  $A$  than Tait-Thomas.  
suitable for high cap, qp

## L4: SFG Videos

Already covered in L1: Intro


[4]

## L5: Current Mirror OTA

Common-Source Amp

$$A_{DC} = -\frac{g_m}{g_{ds1} + g_{ds2}}$$
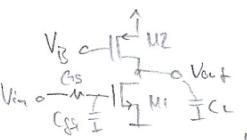
$$A(s) = -\frac{g_m}{g_{ds1} + g_{ds2} + sC_L}$$




$$C_{out} \rightarrow W_{p2} = \frac{g_{ds1} + g_{ds2}}{C_L}$$


$$C_{gs1} \rightarrow W_{p1} = \frac{G_s}{C_{gs1}}$$

Every driving-port impedance of a node with resistive and capacitive components canceled to if gives one pole!


MOS transistor

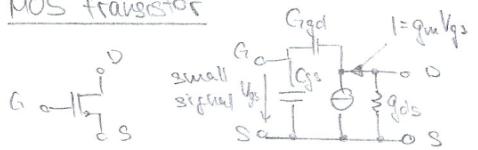

$$g_m \approx 100 \cdot g_{ds}$$

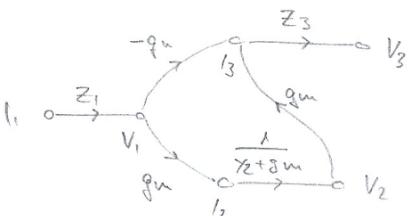

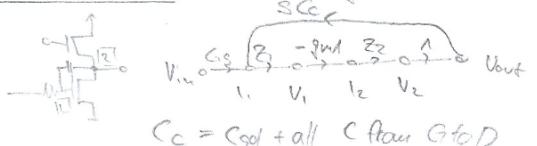Miller Effect caused by  $-H$  from gate to output (in to out)




$$T = -\frac{-G_s(C_{GS} - g_{m1})}{C_{GS}(C_{GS} - g_{m1}) - Y_1 Y_2}$$

pole splitting: increases stability  $\rightarrow$  phase margin  
RHP-zero

$$W_{p1} \approx -\frac{G_1 \cdot G_2}{C_C \cdot g_m}$$


$\rightarrow$  effect of  $C_C$  is multiplied by gain & its load!

OTA

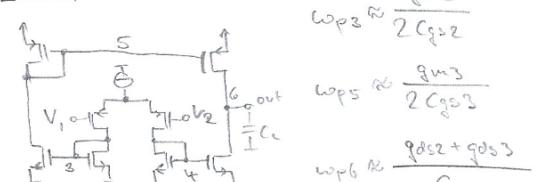

1 for each OP-impedance  
( $Y_3 = Y_4$ )


$$\omega_{25} \approx 2\omega_5$$

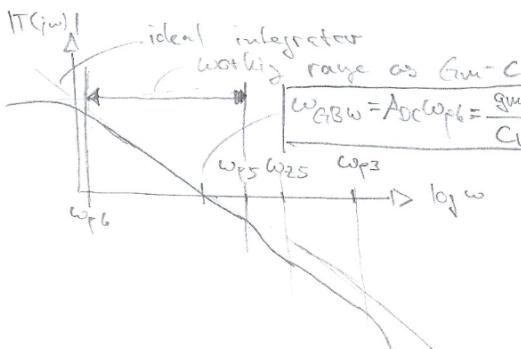

Reducing  $W_{p6}$  ("gain enhancement") [not treated in class]

to reduce  $W_{p6}$  must decrease  $g_{ds2} + g_{ds3} \rightarrow$  cascode transistors (transistors in series)

Regulated cascode (RGC) [not treated]

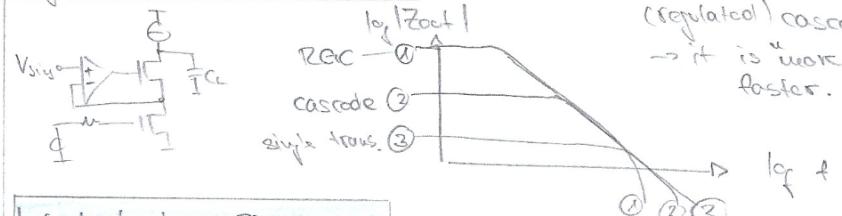


(regulated) cascode more DC gain  
 $\rightarrow$  it is "more stable" faster.
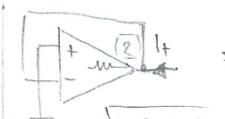
## L6: Inductor Simulation

Opamp with feedback generally opamps are built like

$$V_o = A(V_i - V_2) \quad A = \frac{A_{DC} \omega_0}{s + \omega_0} = \frac{GBWP}{s + \omega_0}$$



$$Z_{out} = \frac{1}{Y_2 + AG_o} \approx \frac{1}{s + \omega_0} \quad \frac{1}{s + \omega_0} \approx \frac{1}{\omega_0 A_{DC} \omega_0} \quad \log \omega$$

$\sqrt{\text{Output of any opamp with FB}}$  is inductive over wide range

3 approximations for  $A$ :  $\omega_l = GBWP$

I)  $A \approx \infty$  II)  $A \approx \frac{w_l}{s}$  III)  $A \approx \frac{w_l}{s + w_b}$

Gyrorator

$$Y_{in} = g_m^2 Z = g_m^2 \frac{1}{Y} \quad \text{with } \boxed{Y = \frac{1}{f}} \quad Y_{in} = \frac{g_m^2}{sC} \approx \frac{1}{s \log}$$

std. gyrorator symbol



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 0 & g_m \\ g_m & 0 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

Single transistor [not treated]

$$G = \frac{g_m}{C} \quad Z_{S1} = \frac{sC_p + G}{s(C_p(G_f + g_{ds}) + G(g_{ds} + g_m))} \quad \frac{1}{G} = \frac{1}{f_2}$$

$$\text{pole: } 2\pi f_p = \frac{G(g_{ds} + g_m)}{C_p(G_f + g_{ds}) + G(g_{ds} + g_m)} \quad \text{zero: } 2\pi f_z = \frac{G}{G_f + g_{ds}}$$
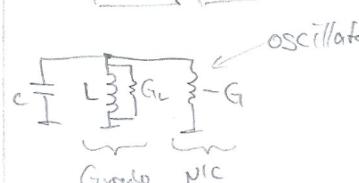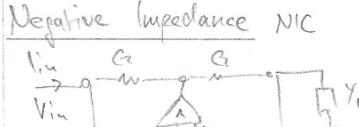
$$A \gg 1 \quad Z_m \approx \frac{G}{G(Y_2 - Y_1)} = -Z_L$$




5

6
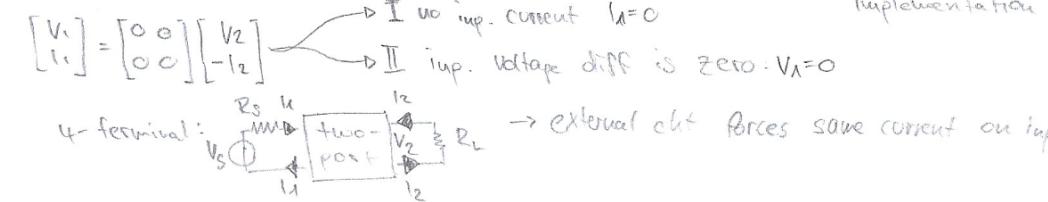
## L7: Current Conveyors


Universal active element (UAE) can build all ccts with this element. Opamp is one implementation of it




Nullors UAE forces 2 eqs but two-port vcts have 3 → unlimited possibilities!  
2-term nets have 1 eqn.

Nullator   $V=0$   $I=0$



Norator   $V$  and 1 arbitrary eqn.

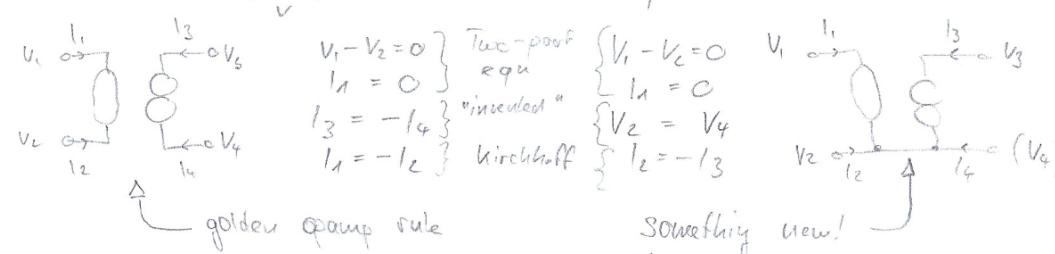




## Current Conveyors

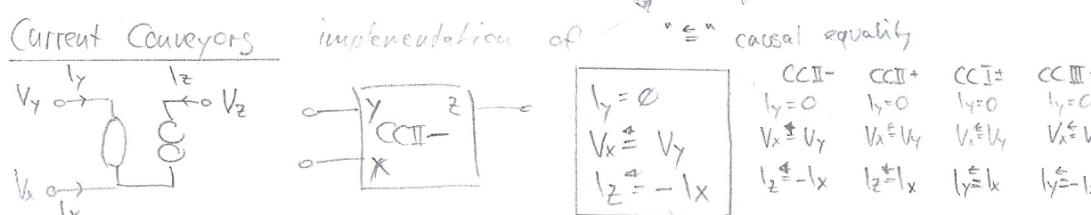

Application CCII+ in CMOS

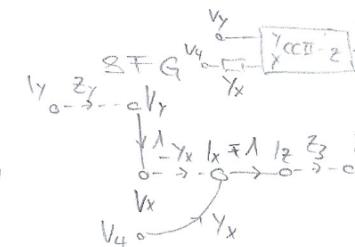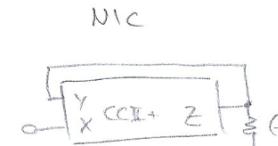


## Voltage vs. Current Feedback

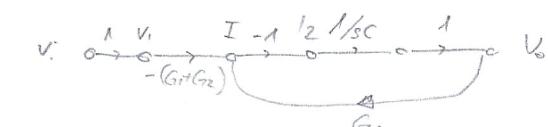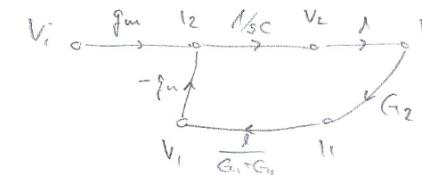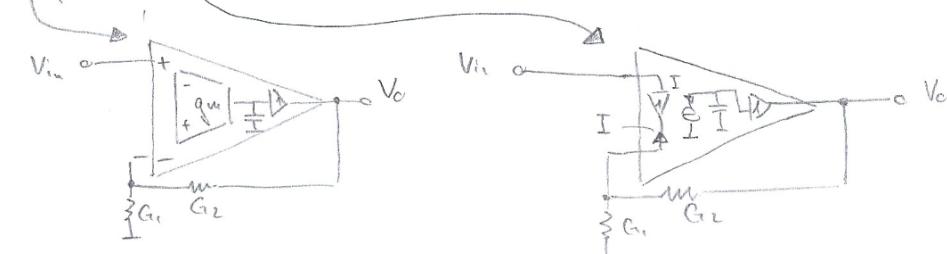

$$A_{DC} = \frac{G_1 + G_2}{G_2} \quad BW = \frac{G_1}{G_1 + G_2} \cdot \frac{g_m}{C}$$


$$A_{DC} = \frac{G_1 + G_2}{G_2} \quad BW = \frac{G_2}{C}$$
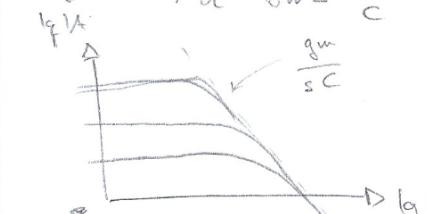
$$GBWP = A_{DC} \cdot BW = \frac{g_m}{C}$$



BW decreases as  $A_{DC}$  increases
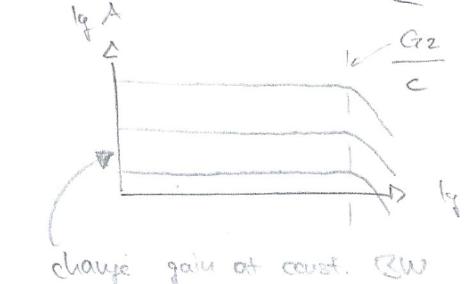
$$GBWP = A_{DC} \cdot BW = \frac{G_1 + G_2}{C}$$



change gain at const. BW

## L8: Quality Measures

### Common & Differential Mode

Common mode:  $V_{\text{cm}} = \frac{V_1 + V_2}{2}$ ,  $V_{\text{d}} = V_1 - V_2$

Symmetrical:  
 $V_i = V_c + \frac{V_d}{2}$        $V_o = V_c - \frac{V_d}{2}$

Differential:  
 $V_c = 0$        $\frac{V_d}{2} \rightarrow V_o = \pm \frac{V_d}{2}$

### Parasitic Gains & Rejection

$$V_o = A_{\text{d}} V_{\text{d}} + A_{\text{c}} V_c + A_{\text{ad}} V_{\text{ad}} + A_{\text{ss}} V_{\text{ss}}$$

$$\text{CMRR} = \frac{1}{A_{\text{c}}} \quad \text{PSRR}_+ = \frac{1}{A_{\text{ad}}} \quad \text{PSRR}_- = \frac{1}{A_{\text{ss}}}$$


$$\frac{1}{\text{CMRR}} + \frac{1}{\text{PSRR}_+} + \frac{1}{\text{PSRR}_-} = 1 \quad \frac{1}{\text{CMRR}} + \frac{1}{\text{PSRR}_+} + \frac{1}{\text{PSRR}_-} = \frac{1}{A_{\text{d}}}$$

If all need to be good, add  $V_{\text{ref}} = 0$  and set  $A_{\text{ref}} = 1 \Rightarrow A_{\text{c}} + A_{\text{ad}} + A_{\text{ss}} = 0$   
(HD)

Harmonic Distortion Any signal through non-linearity  $g(x)$  will give HD

$$g(x) = a_1 + a_2 x^2 + \dots \rightarrow g(A \cos \omega t) = \dots = a_1 A \cos \omega t + \frac{a_2 A^2}{2} \cos 2\omega t + \frac{a_3 A^3}{4} \cos 3\omega t + \dots$$
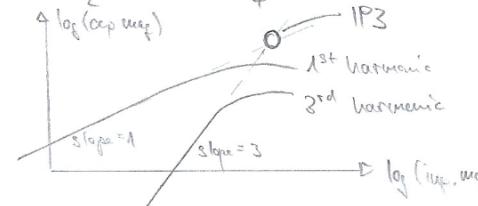
$$\text{HD2} \propto \frac{\frac{a_2 A^2}{2}}{a_1 A} = \frac{A}{2} \cdot \frac{a_2}{a_1}$$





Often small in diff.


largest

IP3: third order intercept point. Complete info about weak-non-linearity of a circuit.

### Measuring HD

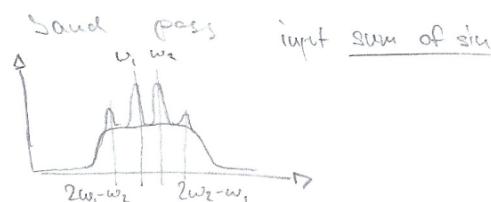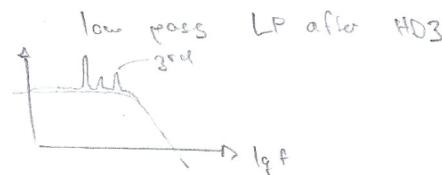

## SNR, dynamic range

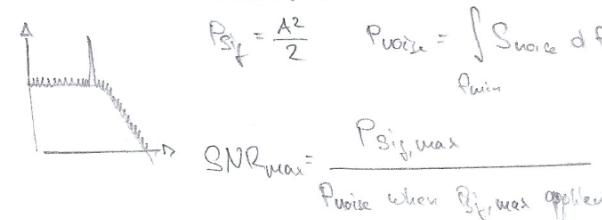

$$P_{\text{sig}} = \frac{A^2}{2}$$

$$\text{Power} = \int_{\text{noise}}^{\text{signal}} \text{Power df}$$

$$\text{SNR} = \frac{P_{\text{sig}}}{\text{Power}}$$

has no meaning if linear, linear not fixed

$$\text{DR} = \frac{P_{\text{sig}, \text{max}}}{P_{\text{sig}, \text{min}}}$$


dep. on application

$$\text{SFDR} = \frac{P_{\text{in}, \text{max}}}{P_{\text{in}, \text{min}}}$$

$P_{\text{in}, \text{min}} = \text{Power} @ \text{no signal}$

$P_{\text{in}, \text{max}} = \text{where } P_{\text{3rd}} = P_{\text{out}} @ \text{no signal}$

## SFDR Spurious-free dynamic range

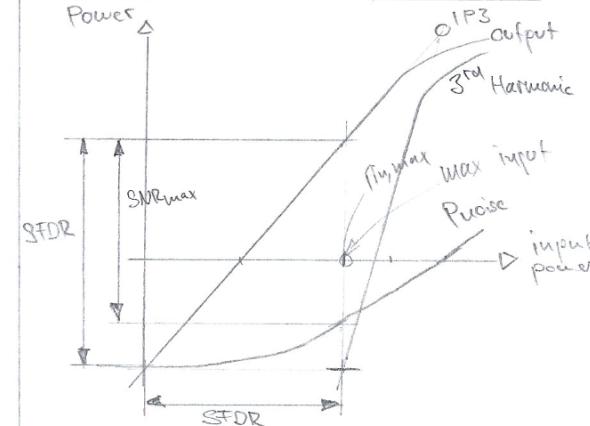

## L9: SC Intro

Resistor:  $\frac{d_1}{C_1} \frac{d_2}{C_2} \rightarrow \frac{d_1}{C_1} \frac{d_2}{C_2} \text{ for } sQ = C(V_1 - V_2)$

$$\phi_1: Q_{C_1} = C_1 V_1$$


$$\phi_2: Q_{C_2} = C_2 V_2$$

$$T = \frac{sQ}{f_S} = f_S C (V_1 - V_2)$$

$$R_{\text{eq}} = \frac{1}{f_S C}$$


$$G_{\text{op}} = f_S C$$

This ratio in CMOS is accurate


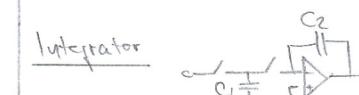


$$T = \frac{1}{f_S} \cdot \frac{C_1}{C_2}$$

Parasitic insensitive problem

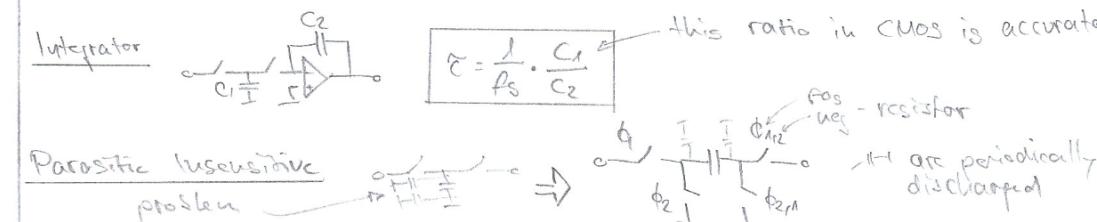

## L10: SC SFG

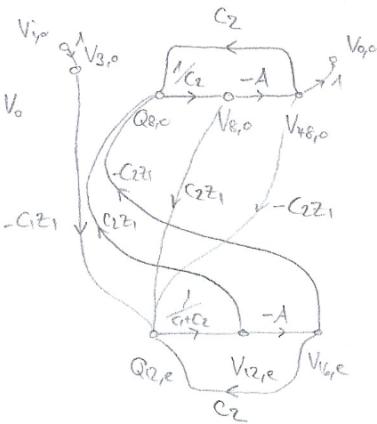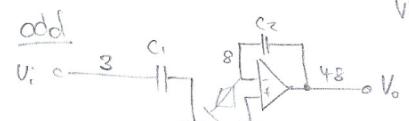

- ① Label nodes as powers of 2
- ② Draw 2x, once odd closed, even else
- ③ Add node table's for closed switches
- ④ For e/o draw driving-point capacitances where required:  $Q \xrightarrow{1/C} 0V$
- ⑤ Label values o/e
- ⑥ Add in & out
- ⑦ Add actives
- ⑧ Add passives

(8) Add charge transfers e->o and o->e

$$\text{e.g. } \frac{3}{12} \xrightarrow{\text{H}} \frac{4}{12} \xrightarrow{\text{H}} V_{3,0} \xrightarrow{C_1} Q_{4,e}$$


\*  $Z_1$  is  $\frac{1}{2}$  cycle

$\rightarrow$  replace  $z^{-2}$  with  $z^{-1}$
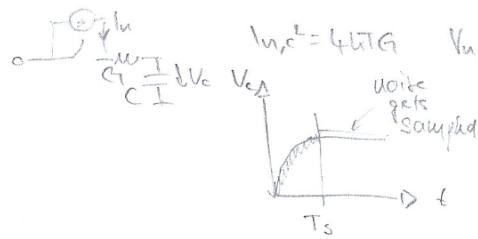
## L11: SC offset & noise

OPAMP offset node  $V_{offs}$   $\xrightarrow{A}$  to opamp offset  $\rightarrow T_{off} = \frac{V_{out}}{V_{offs}}$

SC noise  $C$  is not noisy but switch has  $Q$  that contributes noise



$$V_{n,dc} = 4UTG \quad V_{n,ac} = \frac{4UT}{G}$$

$$V_n = \frac{I_n}{G+SC} = V_n \frac{1}{1+\frac{SC}{G}}$$

$$V_{n,ac}^2 = \int V_n^2 dt / df \propto$$

$$\text{Simple analysis: } E_c = \frac{V_o^2}{2C} \quad E_M = \frac{UT}{2} \Rightarrow E_c = E_M \Rightarrow \boxed{V_{n,ac}^2 = \frac{UT}{C}}$$

Higher  $C$  = less noise power.



## SC filter synthesis [not treated]

One way: take RC circuit & replace  $R$  with SC  $\rightarrow$   $\frac{1}{1+T}$

$\rightarrow$   $T$  becomes periodic in  $f_s$ ,  
 $\rightarrow$  only accurate in low frequencies
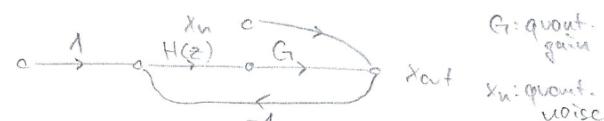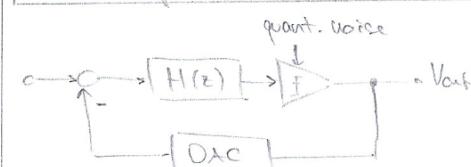
## L12 Sigma-Delta Modulation

$\Sigma\Delta$  Main idea: ADC are subject to quantization noise.  $\Sigma\Delta$  introduces feed-back, such that a different TF is applied to the input and the quant. noise



$$H_{sig} = \frac{X_{out}}{X_{in}} = \frac{H(z)}{1+H(z)}$$

for  $H(z)$  integrator

$$H_{noise} = \frac{X_{out}}{X_{in}} = \frac{1}{1+H(z)}$$

$$H_{sig} = z^{-1}$$


$\leftarrow$  delay  $\rightarrow$  LP

$$H_{noise} = 1-z^{-1} \quad \leftarrow \text{differentiator} \rightarrow \text{HP}$$

### Quantization

$$\text{Signal: sine } V_{rms} = \frac{V_{ref}}{2} \cdot \frac{1}{\sqrt{2}} \quad \text{Noise: } V_{n,rms} = \frac{V_{ref}}{2^N} \cdot \frac{1}{\sqrt{12}} \Rightarrow \boxed{\text{SQNR} = N \cdot 6.02 \text{ dB} + 1.76 \text{ dB}}$$

### Oversampling

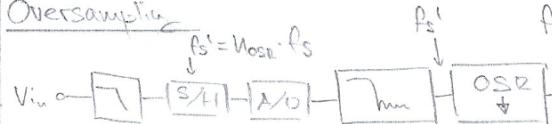


① AA filter needs not to be sharp

②  $V_{rms}^2$  noise power is voice spread over larger range

$$\text{SNR} = N \cdot 6.02 \text{ dB} + 1.76 \text{ dB} + 10 \log(\text{OSR}) \rightarrow \text{win } \frac{1}{2} \text{ per octave of oversampling}$$

### Q-noise shaping

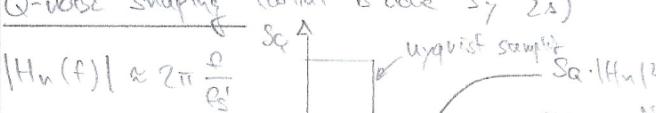

$$P_Q \approx \frac{V_{n,ac}^2}{12} \frac{\pi^2}{3} \text{ noise } V_{n,ac} \gg 1$$

$$\boxed{\text{SNR} = N \cdot 6.02 \text{ dB} + 1.76 \text{ dB} - 5.17 \text{ dB} + 20 \cdot \log \text{ noise}}$$

$\rightarrow$  Noise shaping costs  $\approx 1$  bit but 1.5 bits/octave OSR gained.

For k-th order  $\Sigma\Delta$  (=noise shaping)


$\rightarrow$  gain  $(k+\frac{1}{2})$  bits/octave OSR!

$$\boxed{\text{SNR} = N \cdot 6.02 + 1.76 + 10 \log(2k+1) - 20k \log \pi + 10(2k+1) \log \text{ noise}}$$

(for  $k \geq 5$  get unsatisf.)


## L13: Higher Order $\Sigma\Delta$

1st to 2nd order

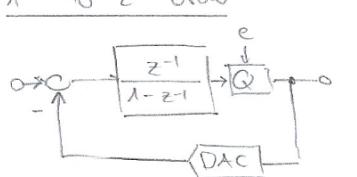

can move  $z^{-1}$  to after part of loop, still stable.
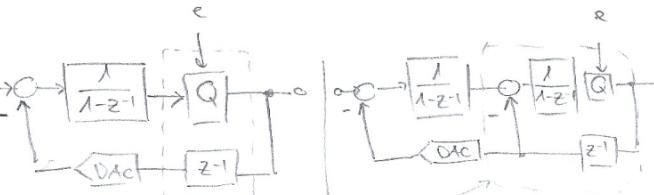
$$T_{sig} = z^{-1} \quad T_u = 1 - z^{-1}$$




any circuit that goes from high to low res, e.g.  $\Sigma\Delta$ !

$$T_{sig} = 1 \quad T_{noise} = 1 - z^{-1}$$

2nd order noise shaper  
↓

$$T_{sig} = 1 \quad T_{noise} = (1 - z^{-1})^2$$

## Multibit Quantizer

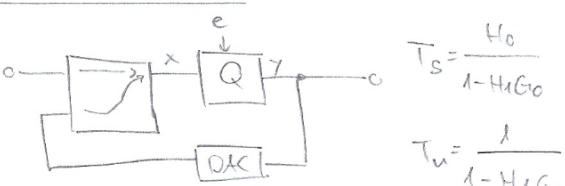

$$T_s = \frac{H_0}{1 - H_0 G_0}$$

$$T_u = \frac{1}{1 - H_0 G_0}$$

$$\begin{aligned} \text{SQNR} = & N \cdot 6.02 \text{ dB} \\ & + 1.76 \text{ dB} \\ & + N \log(2k+1) - 2kh \log \pi \\ & + hC(2k+1) \log \text{MOSR} \end{aligned}$$





$G_0$ : quantizer gain

$N$ : quantizer bits  $\rightarrow$  6dB per bit

$k$ :  $\Sigma\Delta$  order  $\rightarrow k + \frac{1}{2}$  bits/Mosr octave

Mosr: oversampling ratio  $\rightarrow 1.5$  bits/Mosr octave
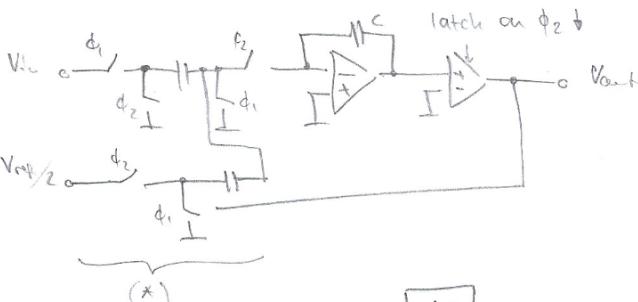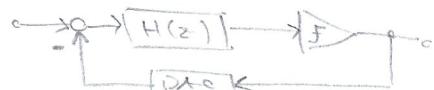
## $\Sigma\Delta$ with switched capacitor




(\*) resistor positive / negative controlled by  $V_{out}$   
 $\rightarrow$  DAC

13
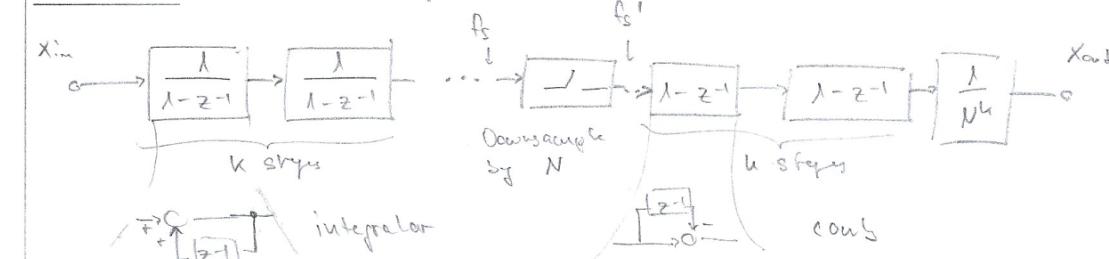
## L14: In and out of $Z\Delta$

CIC filter cascaded integrator comb (or Hopfweiler filter)



integrator

- solve as  $N$  moving average  
- low pass linear phase

$$H(z) = \frac{1}{N^k} \cdot \left( \frac{1 - z^{-N}}{1 - z^{-1}} \right)^k$$

14